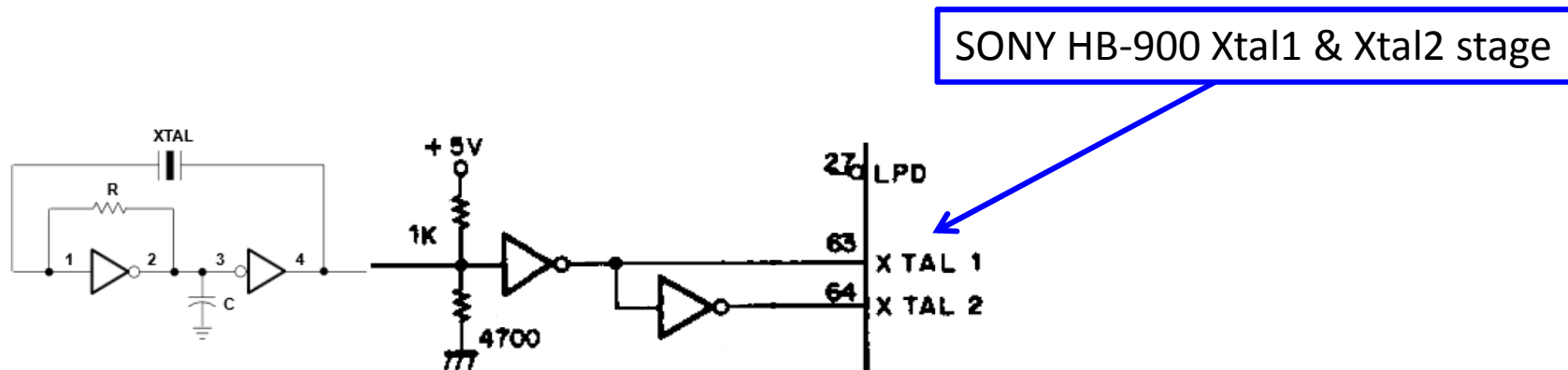


MSX Village VSU/VDU project

Project synoptic

Oscillator schematic



One oscillator that supply all the V99x8 with Xtal1 and Xtal2 signal.
This way the clock is the same for all of them.

CONNECTING ALL VDP

